

## UNIT-1

1) Explain the Ohm's law and limitations

A) Ohm's law and Limitations:

At constant temperature the current flow in element (or) conductor is proportional to potential difference (or) voltage.

(or)

At constant temperature the voltage is directly proportional to current.

$$V \propto I \quad \rightarrow (1)$$

$$V = IR \quad \rightarrow (2)$$

Where,

R = Resistance

From eqn ②

$$I = \frac{V}{R} \quad \rightarrow (3)$$

From eqn ②

$$R = \frac{V}{I} \quad \rightarrow (4)$$

DC power (P)

$$P = V \times I \quad \rightarrow (5)$$

sub eqn ③ in ⑤

$$P = IR \times I$$

$$P = I^2 R \quad \rightarrow (6)$$

Sub eqn ③ in ⑤

$$P = V \times \frac{V}{R}$$

$$P = \frac{V^2}{R}$$

→ (7)

Limitations of law :-

- 1) It is not applied for non-linear elements.
- 2) It is not applied for variable temperature elements.
- 3) Explain the Kirchoff's current law?

A) Kirchoff's law :-

- 1) Kirchoff's current law.
- 2) Kirchoff's voltage law.

Kirchoff's current law :-

At any junction (or) Node the Algebraic sum of incoming current is equal to the Algebraic sum of outgoing current.



(Or)

The Algebraic sum of currents at mode (or) Junction is equal to zero

Mode (or) Junction :-

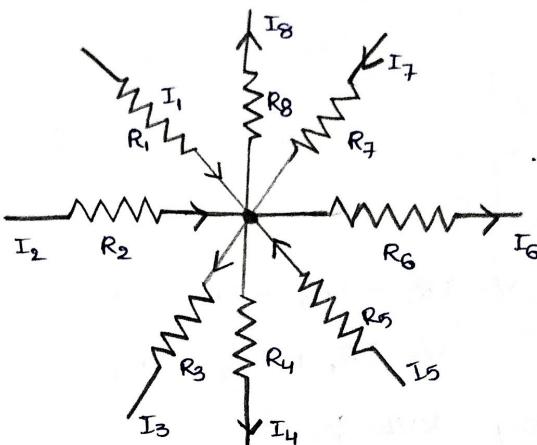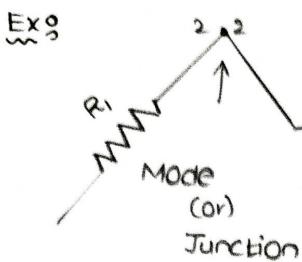Two (or) more Resistors are connected in common point is known mode (or) Junction.





$$I_1 + I_2 + I_5 + I_7 = I_3 + I_4 + I_6 + I_8$$

$$\sum I = 0$$

$$I_1 + I_2 + I_5 + I_7 - I_3 - I_4 - I_6 - I_8 = 0$$

3) Explain the Kirchoff's voltage law ?


A) Kirchoff's voltage law :-

It states that at any loop (or) mesh

The Algebraic sum of Voltage source is equal to the Algebraic sum of voltage drops in the loop.

(or)

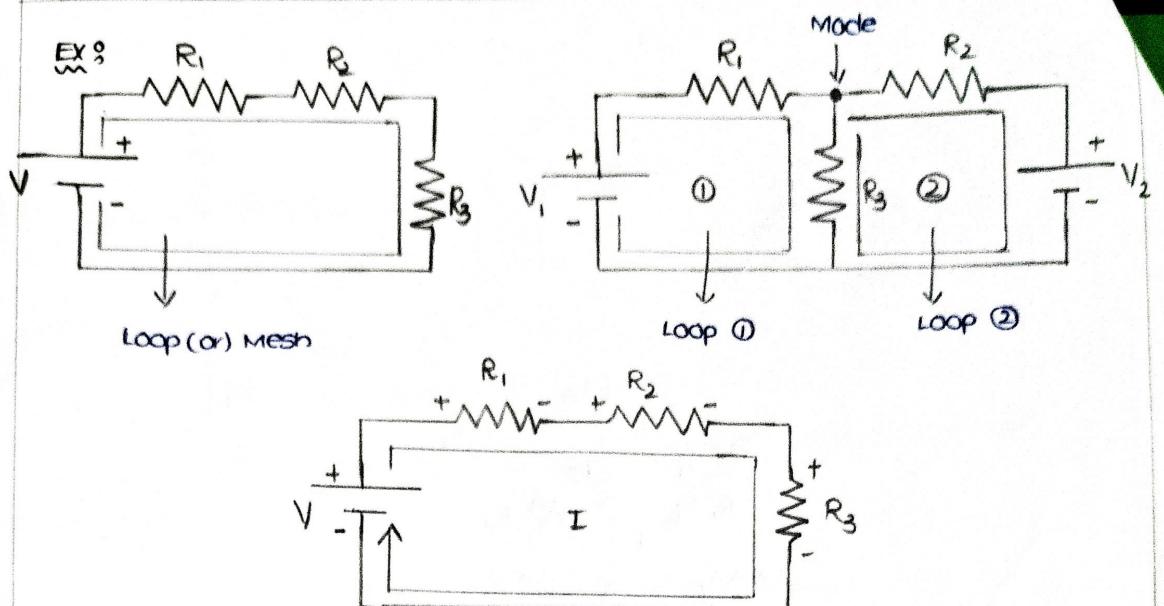At any loop (or) mesh the Algebraic sum of voltage source and voltage drops is equal to zero.



$$V - IR_1 - IR_2 - IR_3 = 0$$


$$V = IR_1 + IR_2 + IR_3$$

Steps for Apply KVL :-

- 1) Identifying the loop.
- 2) Mark the loop current direction.
- 3) Mark the Branch current direction.
- 4) Apply KVL and find the loop currents.

### Problems

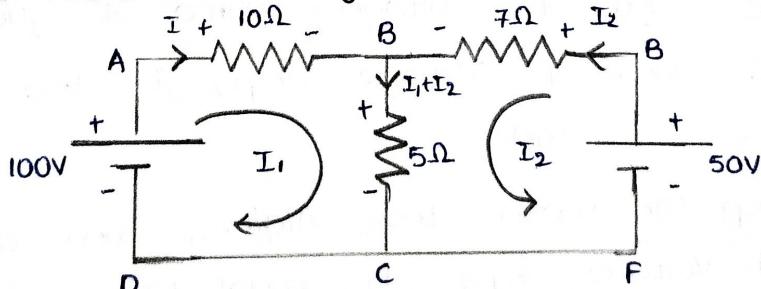- i) Find the loop currents and also power dissipated by  $5\Omega$  resistor for given circuit.



SOL  
Loop ① = ABCDA

$$V = IR$$

Loop ② = BEFcB

$$V = I \cdot 10 = 10I$$

KVL for loop ①

$$+100 - 10I_1 - 5(I_1 + I_2) = 0$$

$$100 - 10I_1 - 5I_1 - 5I_2 = 0$$

$$100 = 10I_1 + 5I_1 + 5I_2$$

$$15I_1 + 5I_2 = 100 \quad \text{--- (1)}$$

KVL for loop ②

$$+50 - 7I_2 - 5(I_1 + I_2) = 0$$

$$50 - 7I_2 - 5I_1 - 5I_2 = 0$$

$$50 = 7I_2 + 5I_1 + 5I_2$$

$$5I_1 + 12I_2 = 50 \quad \text{--- (2)}$$

$$15I_1 + 5I_2 = 100$$

$$5I_1 + 12I_2 = 50$$

$$\begin{bmatrix} 15 & 5 \\ 5 & 12 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 50 \end{bmatrix}$$

$$[R][I] = [N]$$

$$I_1 = 6.12A$$

$$I_2 = 1.61A$$

$$P = I_1^2 R$$

$$P = I_2^2 R$$


The power dissipated by  $5\Omega$  Resistor

$$P = V \times I$$

$$P = V^2 / R$$

$$\begin{aligned}
 P &= I^2 \times R \\
 I \text{ is } 5\Omega \text{ Resistor} &= I^2 R \\
 &= (I_1 \times I_2)^2 R \\
 &= (6.12 + 1.61)^2 \times 5 \\
 &= (7.73)^2 \times 5 \\
 &= (7.73 \times 7.23 \times 5) \\
 &= 298.76 \text{ Watts.}
 \end{aligned}$$

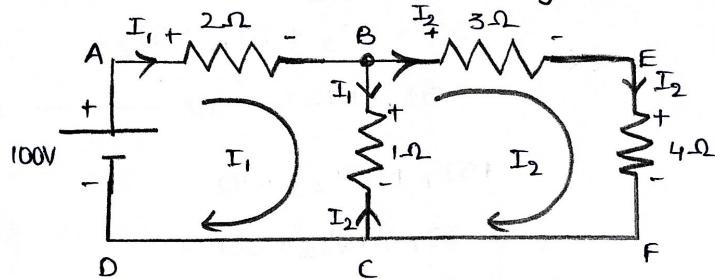- 2) Find the loop currents and also find voltage drop across the resistors for given network.



Loop ① = ABCDA

Loop ② = BEFCB

KVL for Loop ①

$$+100 - 2I_1 - I(I_1 - I_2) = 0$$

$$100 - 2I_1 - I_1 + I_2 = 0$$

$$100 = 2I_1 + I_1 - I_2$$

$$3I_1 - I_2 = 100 \longrightarrow ①$$

KVL for Loop ②

$$-3I_2 - 4I_2 - (I_2 - I_1) = 0$$

$$-3I_2 - 4I_2 - I_2 + I_1 = 0$$

$$0 = 3I_2 + 4I_2 + I_2 - I_1 \\ -I_1 + 8I_2 = 0 \quad \rightarrow (1)$$

$$3I_1 - I_2 = 100 \quad \rightarrow (2)$$

$$-I_1 + 8I_2 = 0 \quad \rightarrow (3)$$

$$\begin{bmatrix} 3 & -1 \\ -1 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 100 \\ 0 \end{bmatrix}$$

$$I_1 = 34.78 \text{ A}$$

$$I_2 = 4.34 \text{ A}$$

1) Voltage across  $2\Omega$  Resistor  $= I_1 R = 34.78 \times 2 = 69.56 \text{ V}$

2) Voltage across  $3\Omega$  Resistor  $= I_2 R = 4.34 \times 3 = 13.02 \text{ V}$

3) Voltage across  $4\Omega$  Resistor  $= I_2 R = 4.34 \times 4 = 17.36 \text{ V}$

4) Voltage across  $1\Omega$  Resistor  $= (I_1 - I_2) \times e$

$$= (34.78 - 4.34) \times 1 = 30.44 \text{ V}$$

4) Explain the superposition theorem ?

A) Superposition Theorem : At any linear and bidirectional network having two (or) more sources (voltage (or) current sources). Then the current in any branch is equal to the algebraic sum of currents in same branch when the sources act as independently.

Steps for solving super position Theorem.

Assume


If voltage sources has short circuit.

If current sources has open circuit.

EAGLE

Then find  $I'$  &  $I''$

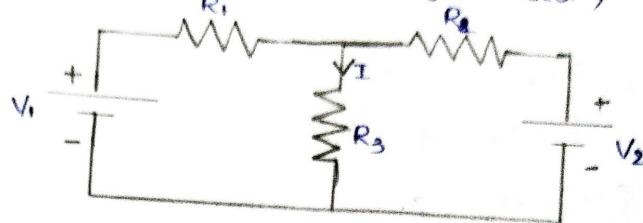
Step 1 :- (Find the  $I$  in  $R_3$  resistor)



Step 2 :- (Find the  $I'$  in  $R_3$  Resistor)

$V_1$  Voltage source is alone and

$V_2$  Voltage source is short circuit.

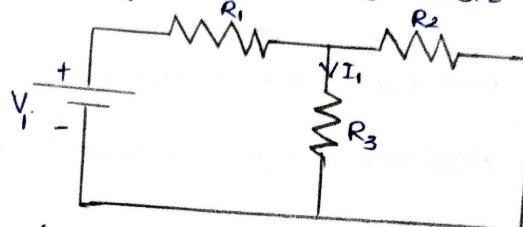

Step 3 :- (To find  $I''$  in  $R_3$  Resistor)

$V_2$  Voltage source is alone and


$V_1$  Voltage source is short circuit

Step 4 :- (Verifying superposition theorem)

$$I = I' + I''$$

Problem

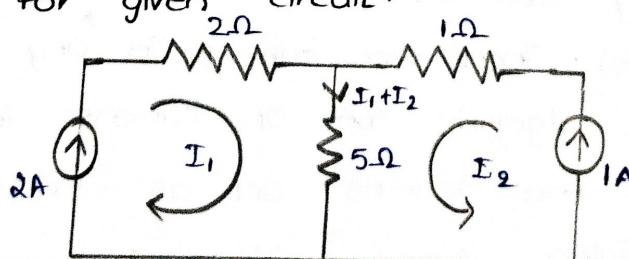- i) Find the current in  $5\Omega$  resistor by using superposition theorem for given circuit.



$$I_1 = 2A$$


$$I_2 = 1A$$

Step 1: (I)

The current in  $5\Omega$  Resistor


$$I = I_1 + I_2 = 2 + 1 = 3A$$

Step 2: (I')

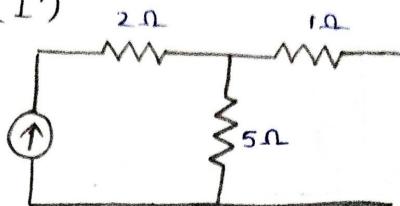

$$I_1 = 2A$$

Step 3: (I'')

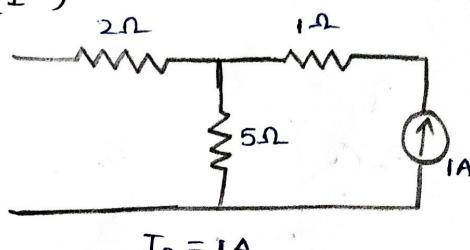





$$I_2 = 1A$$

$$I'' = 1A$$

$$I = I' + I''$$

$$3 = 2 + 1$$

$$3 = 3$$
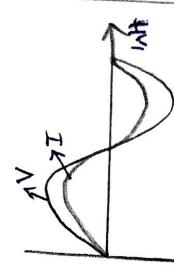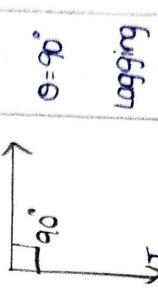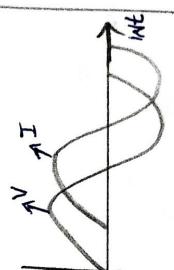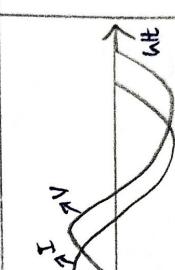
| Parameter        | voltage<br>Elements     | current<br>current               | Avg power                                                            | wave form                                                                          | Phaser diagram                                                                      | Phase angle                    |
|------------------|-------------------------|----------------------------------|----------------------------------------------------------------------|------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------|--------------------------------|
| Resistor<br>$R$  | $V = V_m \sin \omega t$ | $I = I_m \sin \omega t$          | $P_{avg} = \frac{V_m I_m}{2}$<br>(or)<br>$P_{avg} = V_{rms} I_{rms}$ |   |    | $\theta = 0^\circ$             |
| Inductor<br>$L$  | $V = V_m \sin \omega t$ | $I = I_m \sin(\omega t - \pi/2)$ | $P_{avg} = 0$                                                        |   |  | $\theta = 90^\circ$<br>Lagging |
| Capacitor<br>$C$ | $V = V_m \sin \omega t$ | $I = I_m \sin(\omega t + \pi/2)$ | $P_{avg} = 0$                                                        |  |  | $\theta = 90^\circ$<br>Leading |

### Impedance

Concept of impedance & AC power:


Impedance ( $Z$ ):

The impedance is offered by AC current circuit to oppose the flow of current  $I$  in  $\Omega$

$$\bar{V} = \bar{V}_R + \bar{V}_L \quad \text{--- (1)}$$

$$\bar{I}_Z = \bar{I}_R + \bar{I}_{X_L} \quad \text{--- (2)}$$

By using eqn ① to draw

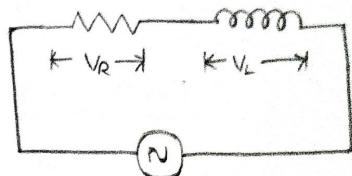

$$V = V_m \sin \omega t$$

### Voltage Triangle:

By Apply Pythagoras theorem

$$V^2 = V_R^2 + V_L^2$$


$$V = \sqrt{V_R^2 + V_L^2}$$

$$\sin \theta = \frac{V_L}{V}$$

$$\cos \theta = \frac{V_R}{V}$$

$$\tan \theta = \frac{V_L}{V_R}$$


$$\theta = \tan^{-1} \frac{V_L}{V_R}$$

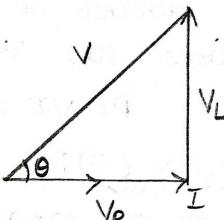

$\theta \rightarrow$  phase angle

### Impedance Triangle

By using eqn ②

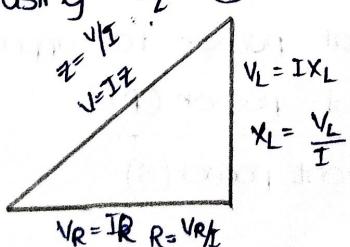

$$Z = \sqrt{R^2 + X_L^2}$$


$$\sin\theta = \frac{X_L}{Z}$$

$$\cos\theta = R/Z$$

$$\tan\theta = X_L/R$$

$$\theta = \tan^{-1} \frac{X_L}{R}$$

Power Triangle

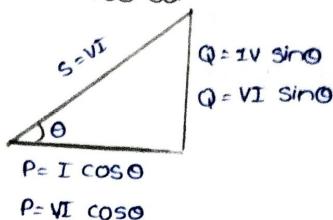

$$P = VI \cos\theta$$

$$P = VI \cos\theta$$

Real Power (P) :-

It is the product of voltage and active component. The units is watts (or) kilo watts.

$$P = VI \cos\theta$$

Reactive Power (Q) :-

It is product of voltage and reactive component. The unit is VAR (or) kilo VAR

$$Q = VI \sin\theta$$

Apparent power (S) :-

It is product of RMS voltage & RMS current

$$S = V_{rms} \times I_{rms}$$

$$S = V_m I_m / 2$$

$$S = V_m / \sqrt{2} \times I_m / \sqrt{2}$$

Power factor ( $\cos\theta$ ) :-

It is the ratio of real power to apparent power

$$\cos\theta = \frac{\text{Real power (P)}}{\text{Apparent power (S)}}$$